

09/03/2024

IFT-1227

Rapport du devoir 2

Tarik Hireche


202 301 89

Ilyesse Bouzammita

202 761 43

 
1. a) Premier circuit

Modélisation comportementale: Convertisseur C à 2 vers DCB




1. b) Deuxième circuit:

Module comportemental: Afficheur DCB

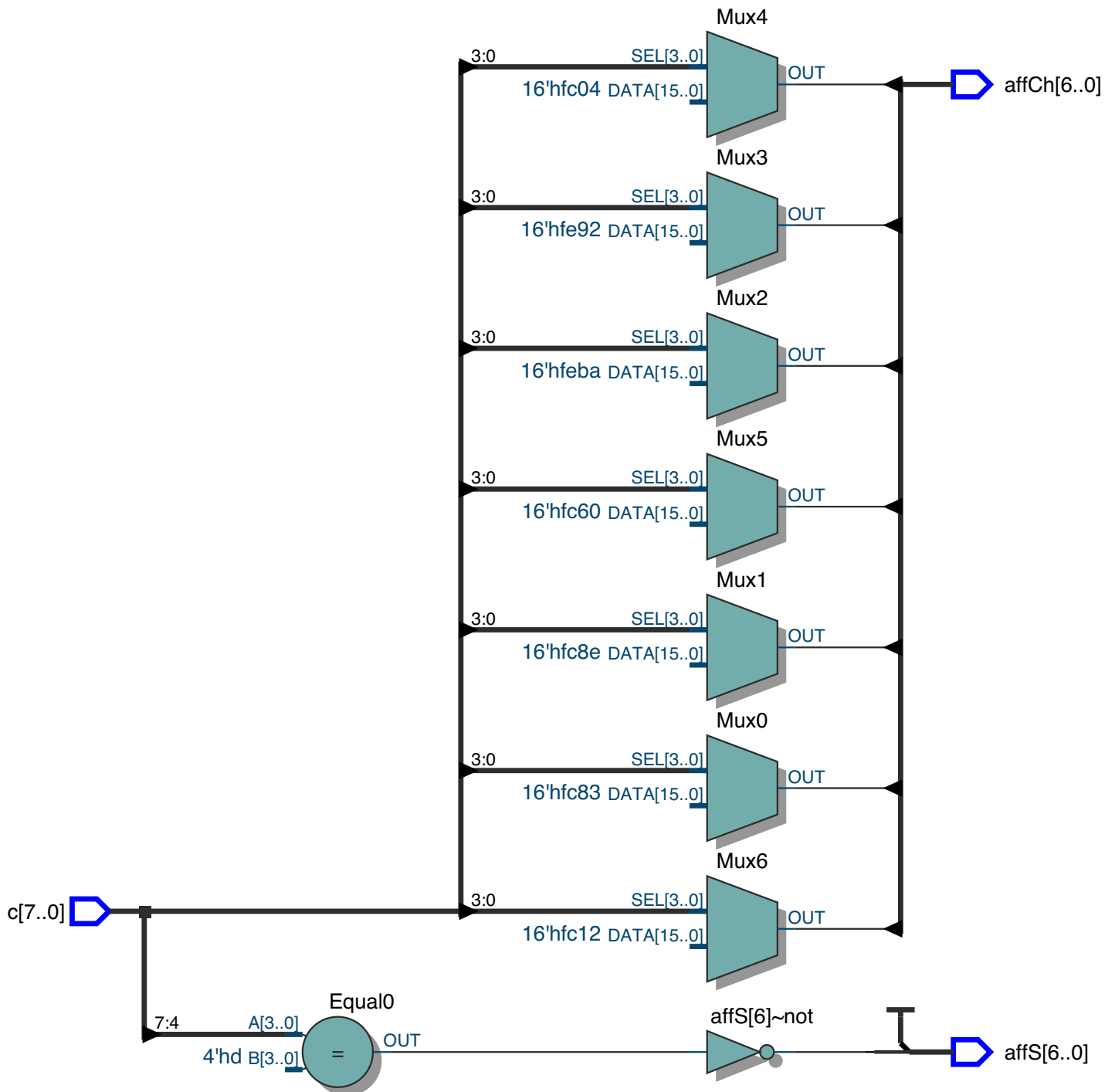


 1.c) Troisième circuit:


Modélisation structurelle du troisième circuit en utilisant les circuits de 1. a) et 1. b):



2. a) Diagramme de transition d'états:

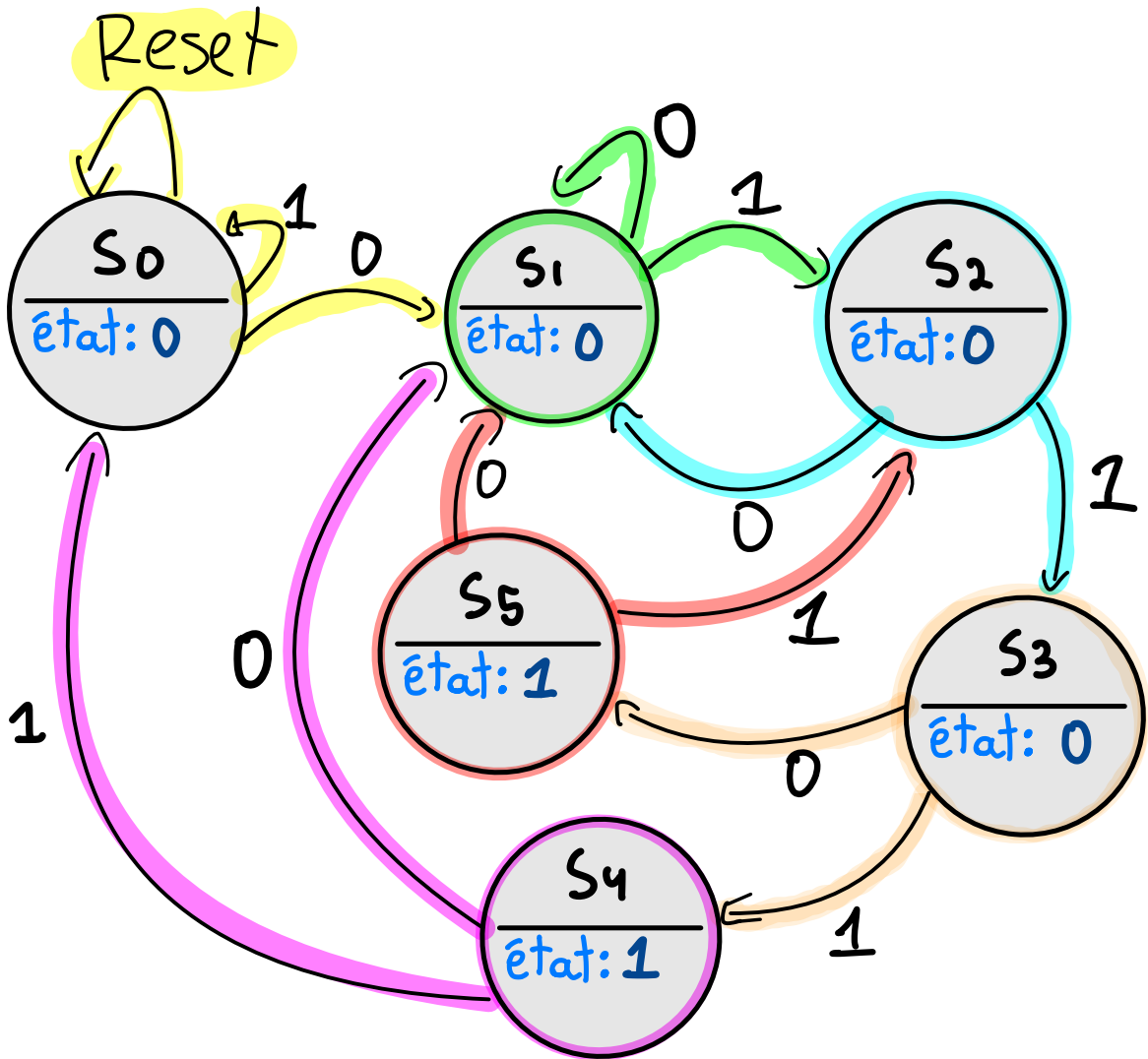

 2. b) Image du circuit synthétisé (MooreFSM):



Capture d'écran TestBench:

```
Transcript
# Loading project Devoir2_sim
# Compile of MooreFSM_tb.vhd was successful.
ModelSim> vsim work.moorefsm_tb
# vsim work.moorefsm_tb
# Start time: 13:59:12 on Mar 12, 2024
# Loading std.standard
# Loading std.textio(body)
# Loading ieee.std_logic_1164(body)
# Loading work.moorefsm_tb(tb_architecture)
# Loading work.moorefsm(fast)
add wave -position insertpoint sim:/moorefsm_tb/*
VSIM 3> run
# ** Note: All tests passed
# Time: 130 ns Iteration: 0 Instance: /moorefsm_tb
VSIM 4>
```

Code testbench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MooreFSM_tb is
end entity;

architecture tb_architecture of MooreFSM_tb is
    component MooreFSM
        port(clk, reset: in STD_LOGIC;
            x: in STD_LOGIC;
            y: out STD_LOGIC);
    end component;

    signal clk, reset, x, y: STD_LOGIC;

begin
    -- Instantiating the MooreFSM component along with its inputs
    and outputs
    dut: MooreFSM port map (
        clk => clk,
        reset => reset,
        x => x,
        y => y);

    -- Clock generation for the FSM
    process
    begin
        clk <= '0';
        wait for 5 ns;
        clk <= '1';
        wait for 5 ns;
    end process;
```

Suite du code



```

-- Test process
process
begin
    -- Initial reset, state to S0
    reset <= '1';
    wait for 10 ns;
    reset <= '0';
    wait for 10 ns;

    -- Test #1: Sequence to check for 0110
    x <= '0'; wait for 10 ns; -- Bit 1 S0 to S1
    x <= '1'; wait for 10 ns; -- Bit 2 S1 to S2
    x <= '1'; wait for 10 ns; -- Bit 3 S2 to S3
    x <= '0'; wait for 10 ns; -- Bit 4, S3 to S4: should match 0110
    assert y = '1' report "Test for sequence 0110 failed";

    -- Reset again to S0 for the next test
    reset <= '1';
    wait for 10 ns;
    reset <= '0';
    wait for 10 ns;

    -- Test #2: Sequence to check for 0111
    x <= '0'; wait for 10 ns; -- Bit 1 S0 to S1
    x <= '1'; wait for 10 ns; -- Bit 2 S1 to S2
    x <= '1'; wait for 10 ns; -- Bit 3 S2 to S3
    x <= '1'; wait for 10 ns; -- Bit 4, S3 to S5: should match 0111
    assert y = '1' report "Test for sequence 0111 failed";

    -- Reset back to S0
    reset <= '1';
    wait for 10 ns;
    reset <= '0';

    report "All tests passed";
    wait;
end process;
end tb_architecture;

```